

AI1110 Hardware Project

Gadekar Shivendraraje Baban(CS22BTECH11022)

In this project we have made a random number generator using Decoder, Clock, 7-seg Display


OUTPUT

Output was changing digits on the seven segment display the output is shown in figure

Component	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K Ω	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

PROCEDURE

- 1) Make connection to the 555 circuit according to diagram(Figure 1).
- 2) Connect the clock output of 555 timer circuit to clock signal of D-Flip Flop.
- 3) Create a circuit for shift registers using D-Flip Flops
- 4) Make connection to the XOR gate or 7486 IC according to the figure 4.
- 5) Connect the decoder 7447 IC as shown in the figure 5.
- 6) Connect 7-seg display to the decoder 7447 IC according to figure 6.
- 7) Make the remaining connections and connect them to a power source.

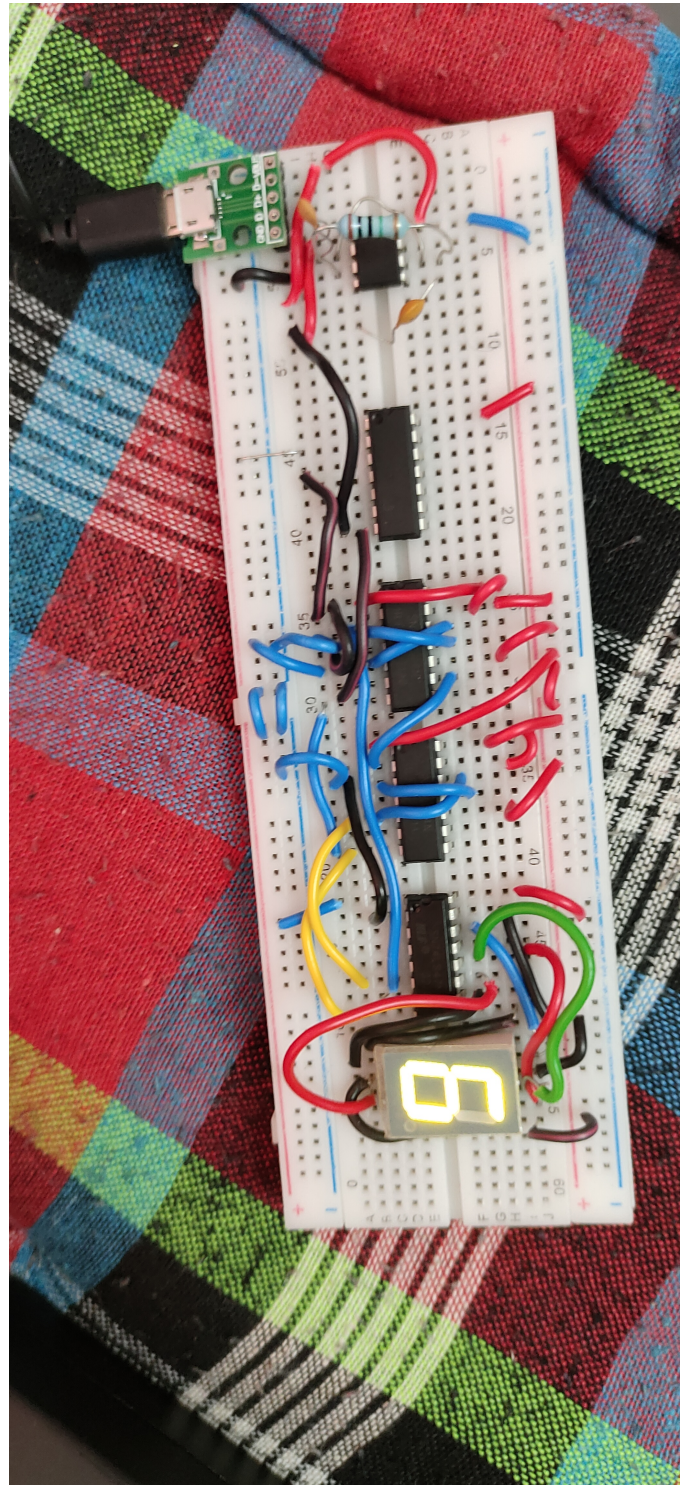

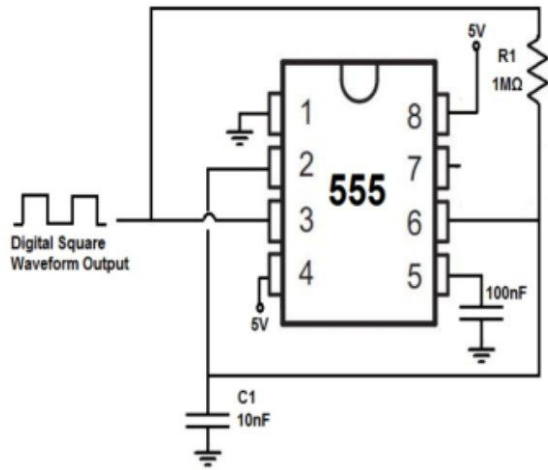


Fig. 1. Connection in 555 timer circuit

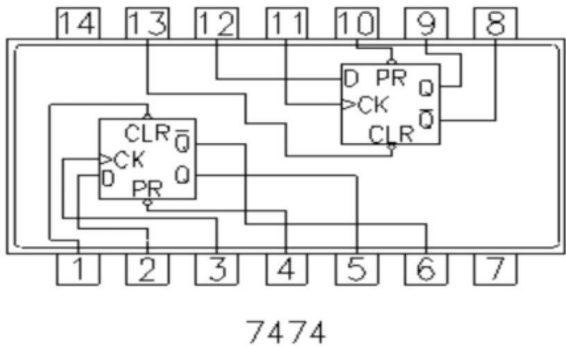


Fig. 3. Connection in 7474 IC

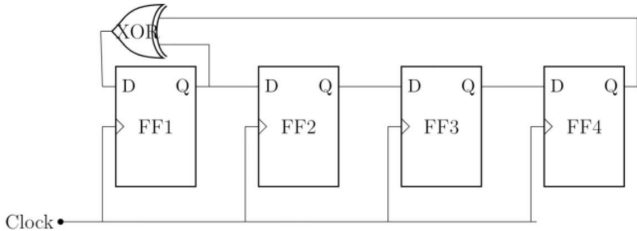


Fig. 4. Connection in XOR gate



Fig. 5. Connection in Decoder gate

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Fig. 6. Connection of seven segmented display with decoder

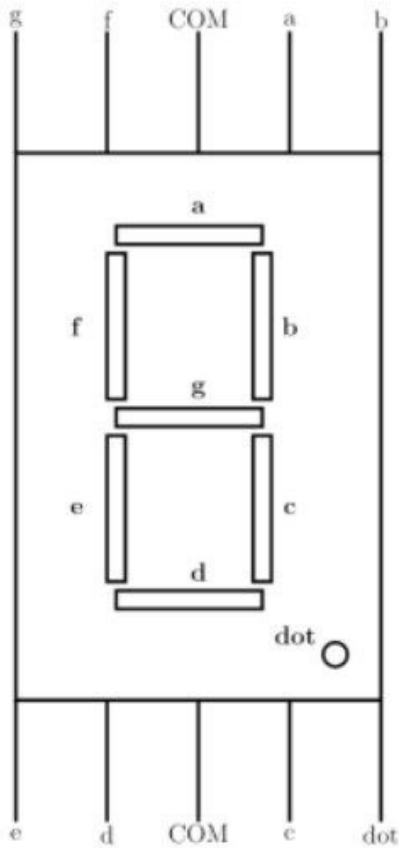


Fig. 6. Seven segmented display